

Basic Circuits Simulations and Practicals

Abhin M (244002)

Prepared Using LT spice

December 8, 2024

Contents

1 PROBLEM A	2
2 PROBLEM B	3
3 PROBLEM C	4
4 PROBLEM D	6
5 PROBLEM E	7
6 PROBLEM F	8
7 PROBLEM G	9
8 PROBLEM H	10
9 PROBLEM I	11
10 PROBLEM J	12

AIM

To solve the given problems and simulate them using LTspice.

1 PROBLEM A

For the circuit given below, determine the output voltage of the circuit.

Solution

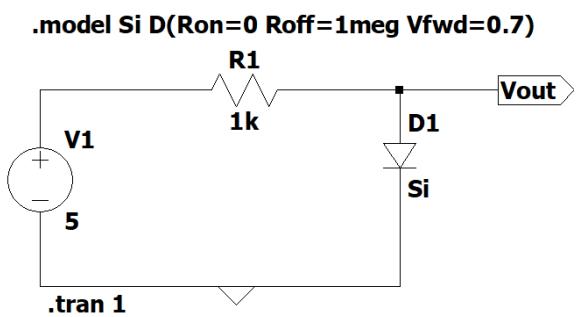


Figure 1: Circuit

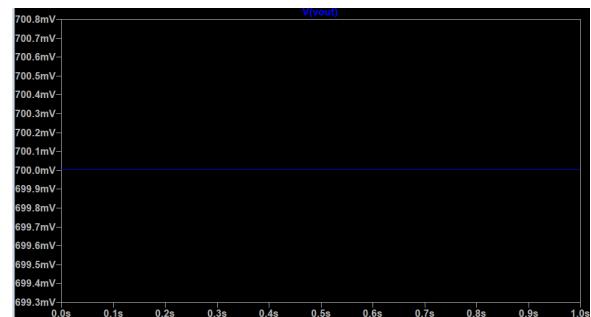


Figure 2: Simulation Output

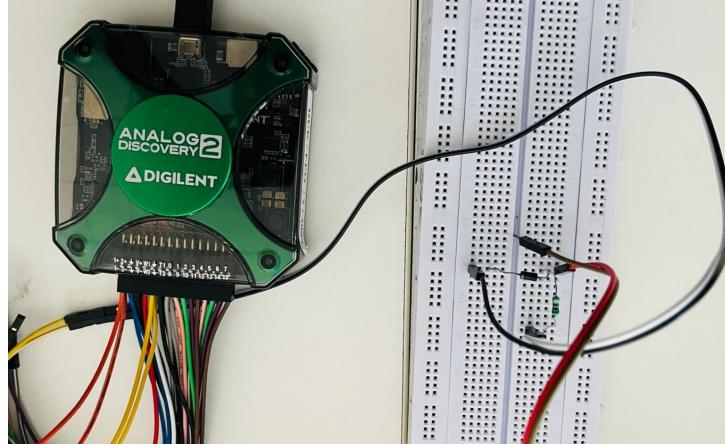


Figure 3: Practical



Figure 4: Practical Output

2 PROBLEM B

For the circuit given below, determine the output voltage of the circuit.

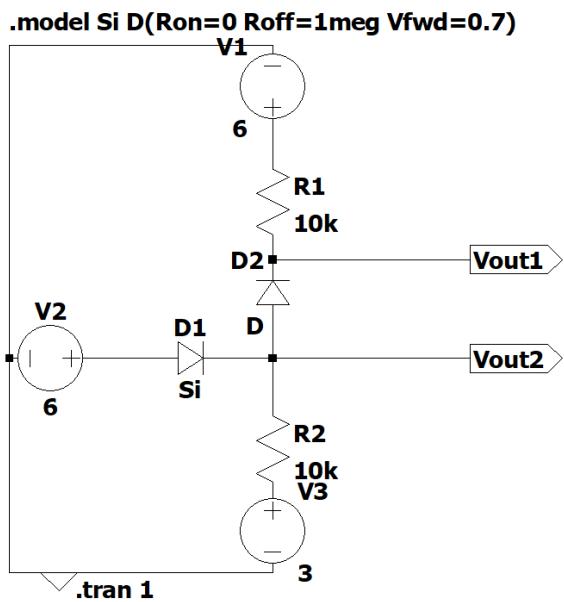


Figure 5: Circuit

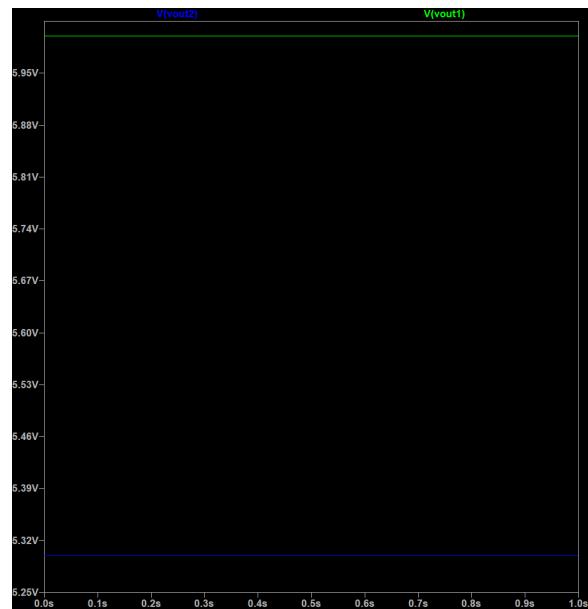


Figure 6: Simulation Output

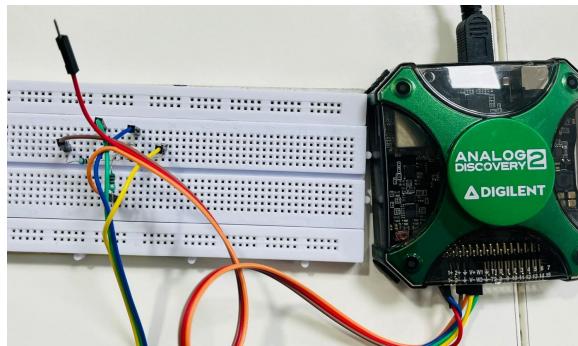


Figure 7: Practical

3 PROBLEM C

Find the diode states and the values of I and V in the circuit given below.


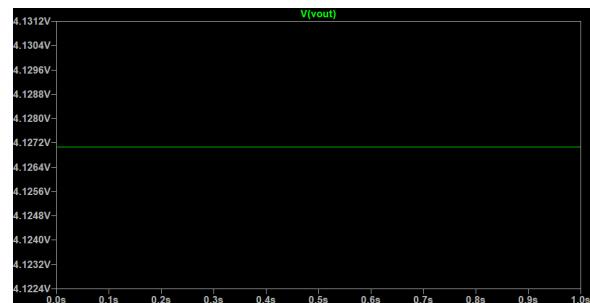


Figure 9: Simulation Output

Figure 8: Circuit

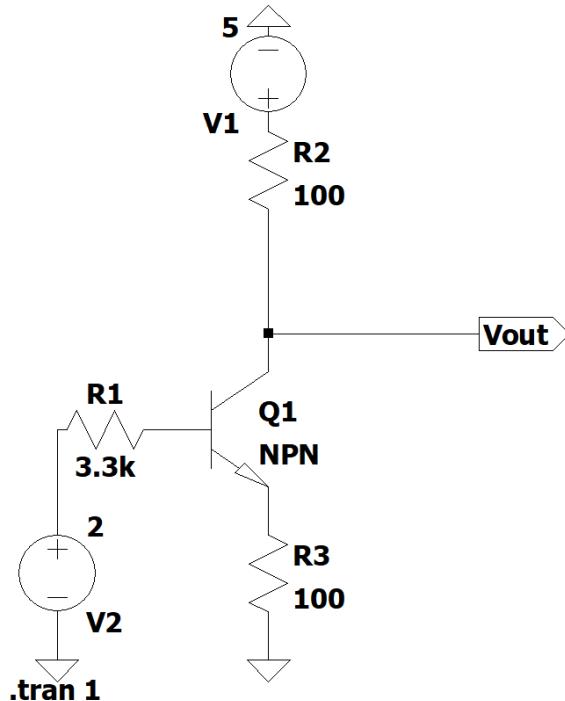

Figure 10: Practical

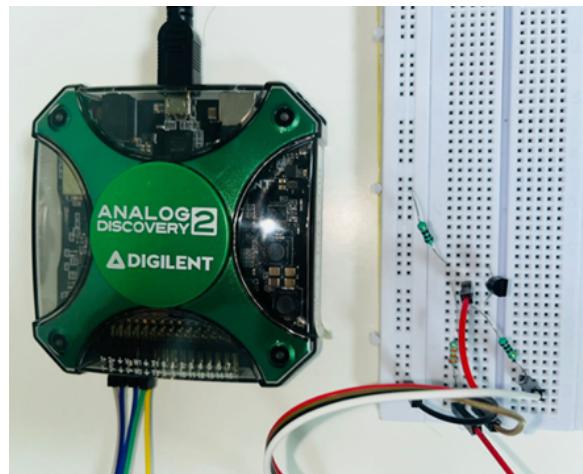


Figure 11: Simulation Output

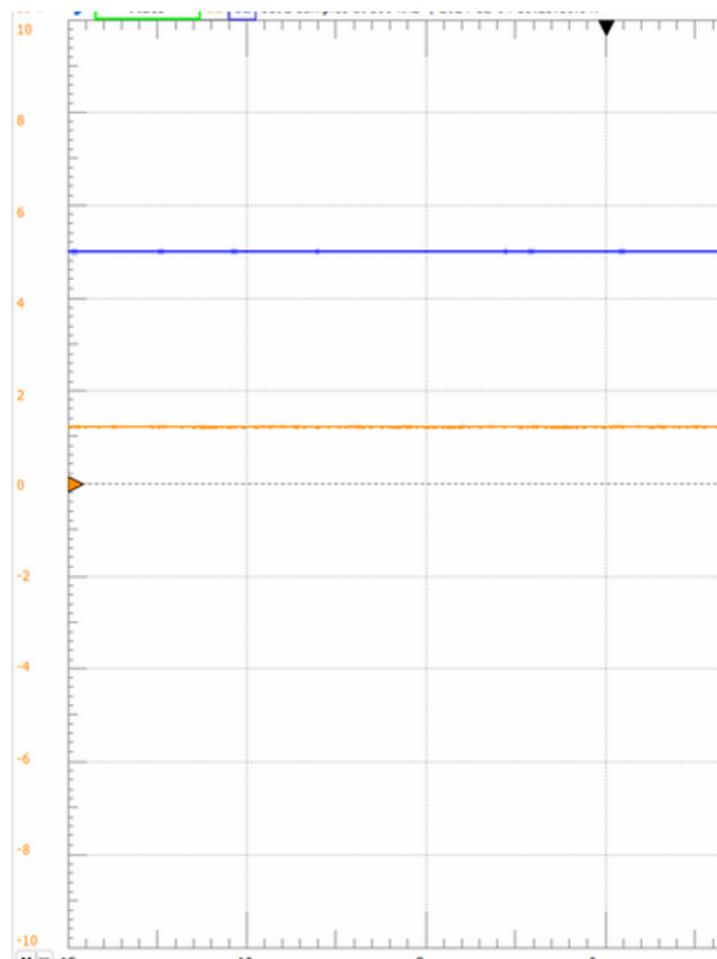


Figure 12: Pratical Output

4 PROBLEM D

For the circuit given below, calculate the output voltage.

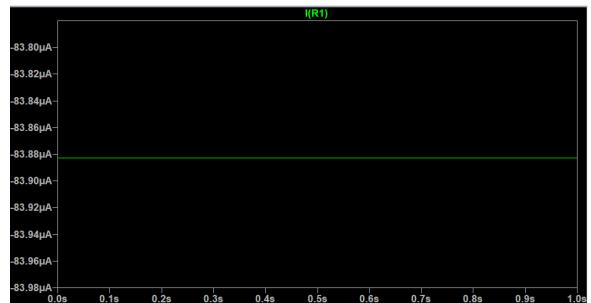
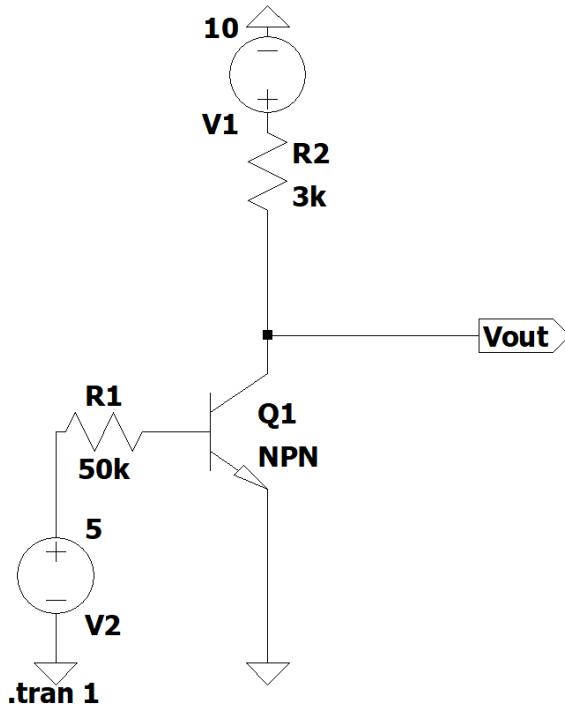


Figure 14: Simulation Output

Figure 13: Circuit

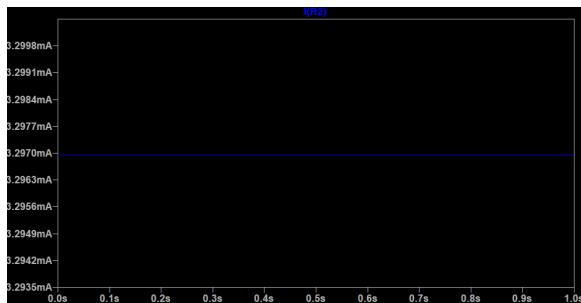


Figure 15: Simulation Output

5 PROBLEM E

For the circuit given below, calculate the output voltage.

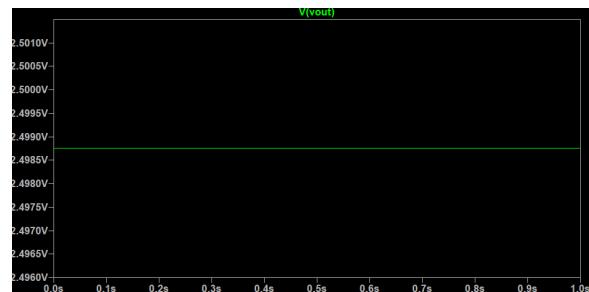
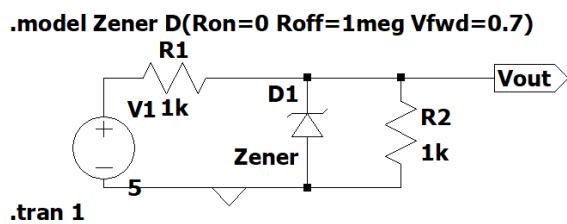


Figure 16: Circuit

Figure 17: Simulation Output

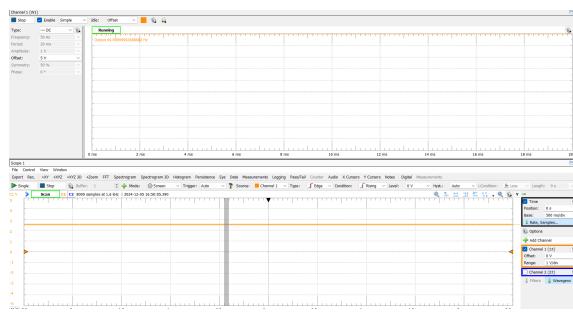


Figure 18: Simulation Output

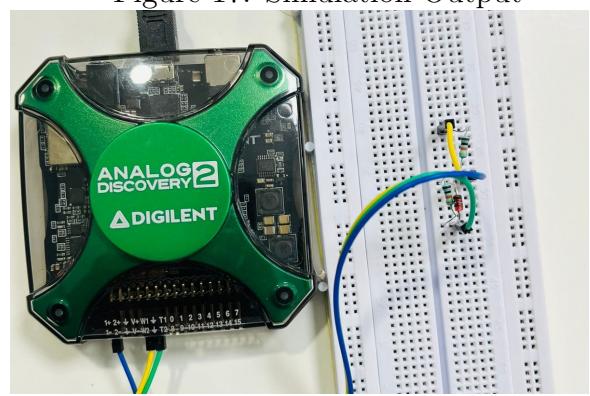


Figure 19: Simulation Output

6 PROBLEM F

Simulate and find the output voltage of the given circuit.

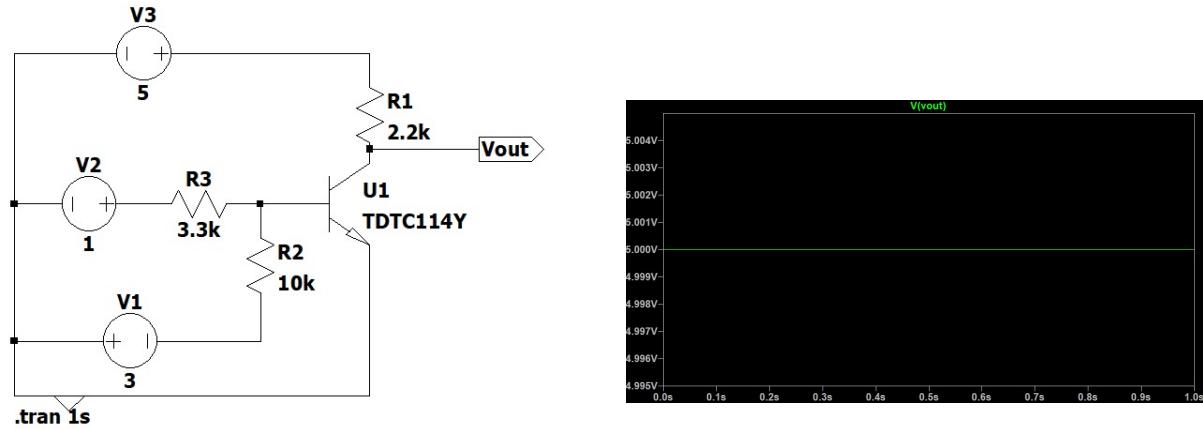


Figure 21: Simulation Output

Figure 20: Circuit

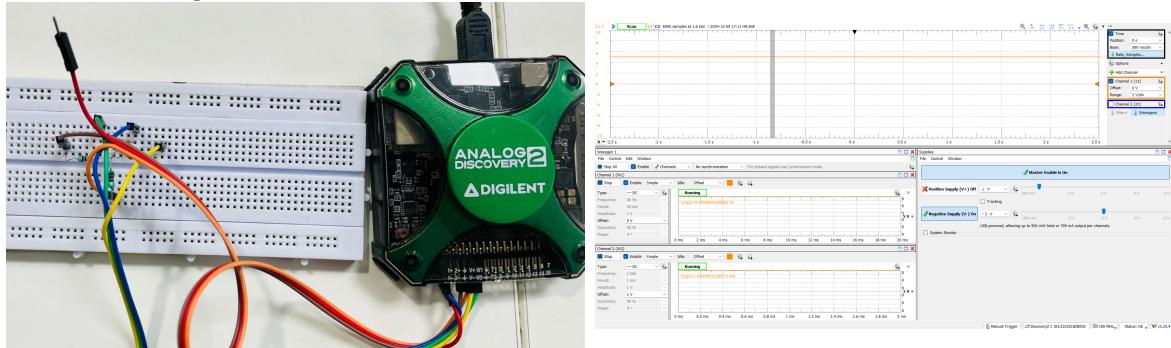


Figure 22: Pratical

Figure 23: Pratical Output

7 PROBLEM G

Analyze the working of this low pass filter

Solutions

A low pass filter will attenuates all the frequency that is about the cut off frequency and pass all the frequency below that

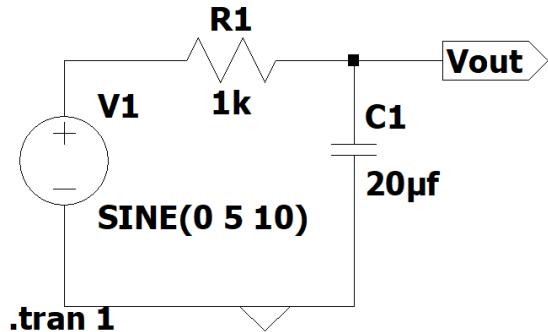


Figure 24: Circuit



Figure 25: Simulation Output

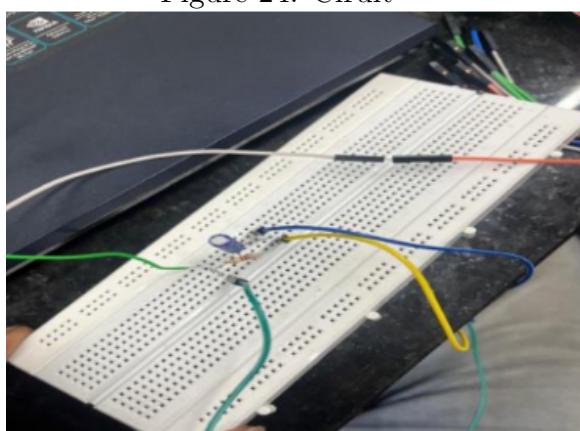


Figure 26: Simulation Output

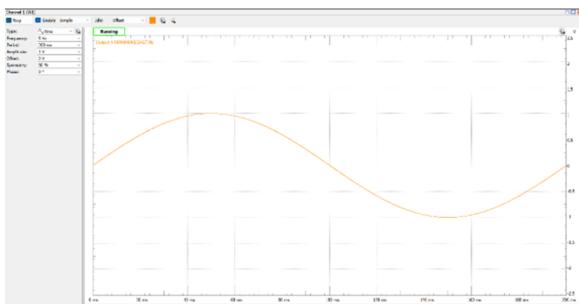


Figure 27: Simulation input

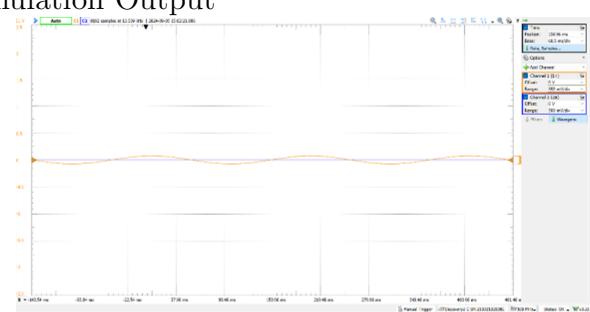


Figure 28: Simulation Output

8 PROBLEM H

Find the output voltage of this given circuit.

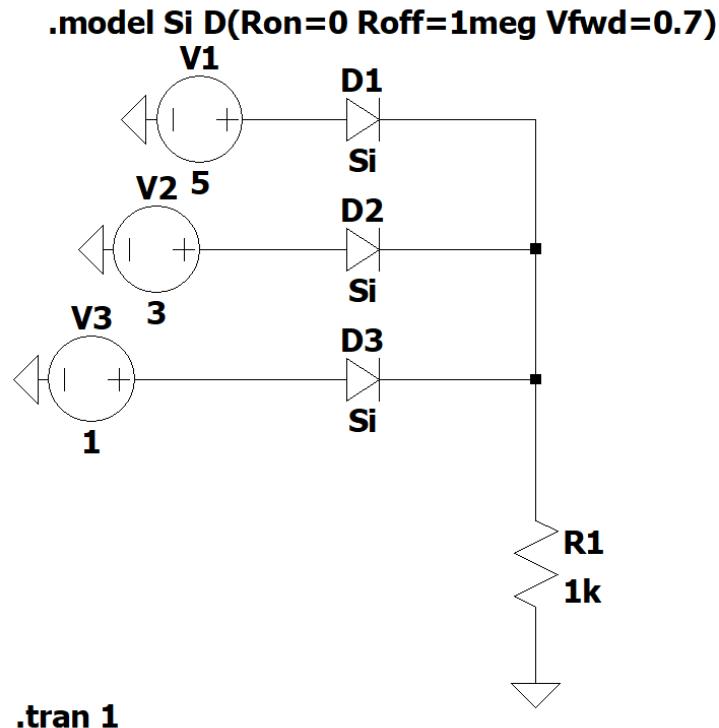


Figure 29: Circuit

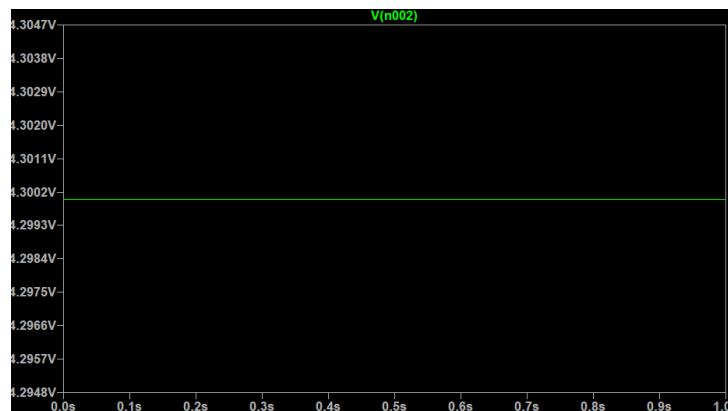


Figure 30: Output

9 PROBLEM I

Design a Positive clipper circuit and show its input and output waveform.

Solutions

A Clipper circuit in which the diode is connected in series to the input signal and that attenuates the positive portions of the waveform, is termed as Positive Clipper.

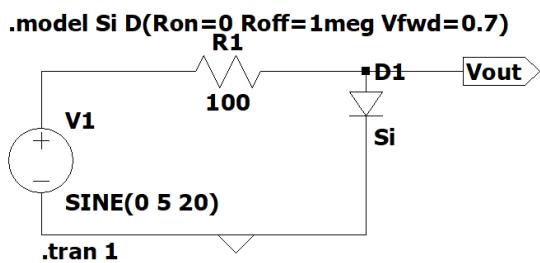


Figure 31: Circuit

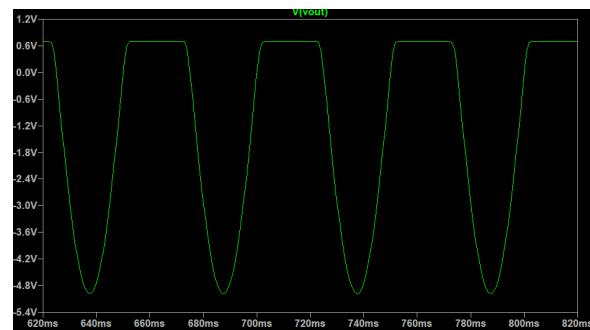


Figure 32: current at collector

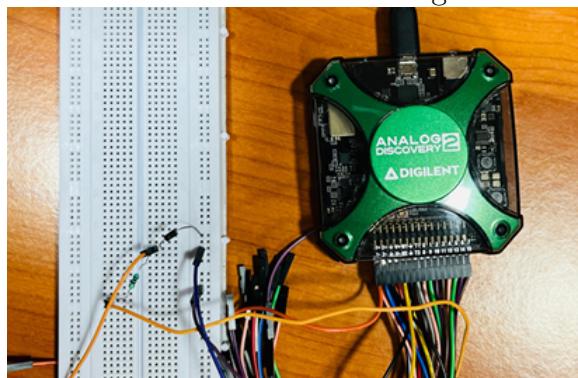


Figure 33: current at collector

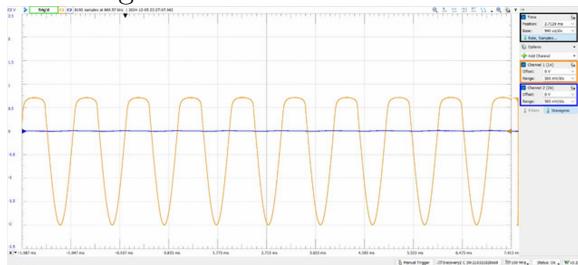


Figure 34: current at collector

10 PROBLEM J

Design a negative clipper circuit and show its input and output waveform.

Solutions

A negative clipper removes the negative portion of an input signal by using a diode and a reference voltage. When the input voltage goes below the reference level, the diode becomes forward-biased, conducting and "clipping" the signal to the reference voltage

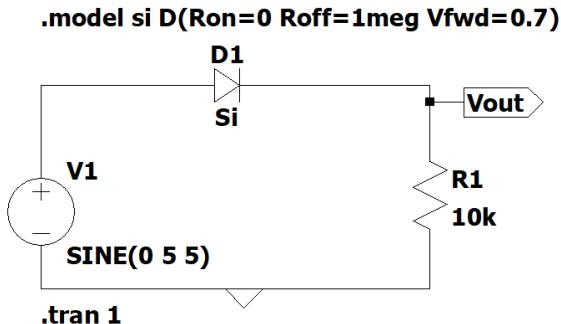


Figure 35: Circuits

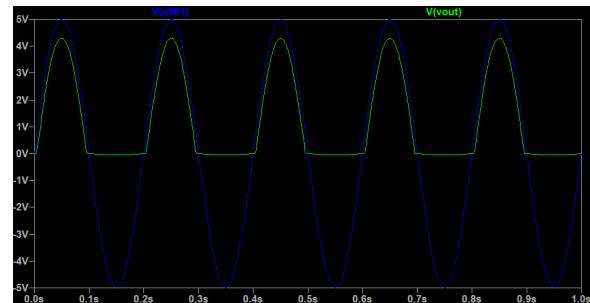


Figure 36: Simulation output

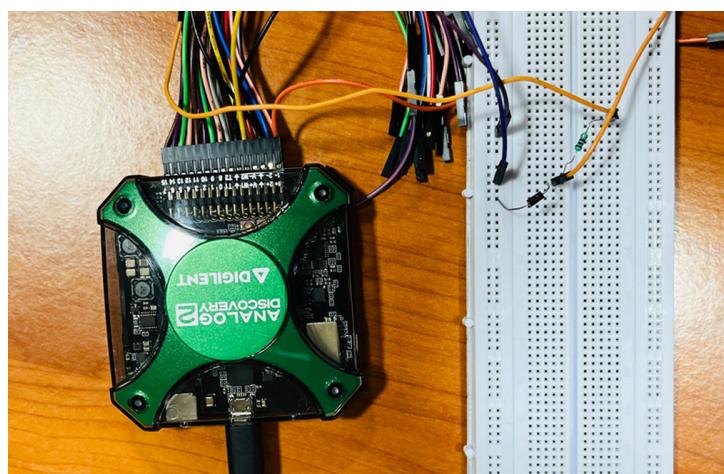


Figure 37: Practical

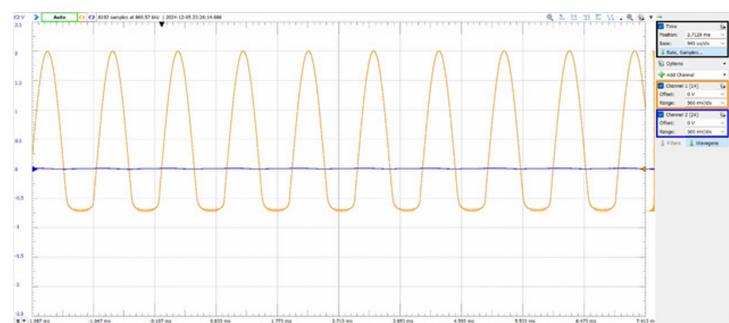


Figure 38: Pratical output